

Binary Adders (Half adder and full adder)

Half Adder:



Specification: 2 inputs (X,Y)
 2 outputs (C,S)

From the verbal explanation of a half adder, we find that this circuit needs two binary inputs and two binary outputs. The input variables designate the augend and addend bits; the output variables produce the sum and carry. We assign symbols x and y to the two inputs and S (for sum) and C (for carry) to the outputs. The truth table for the half adder is listed in Table.


X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

The C output is 1 only when both inputs are 1. The S output represents the least significant bit of the sum.

FIGURE 4.5 Implementation of half adder

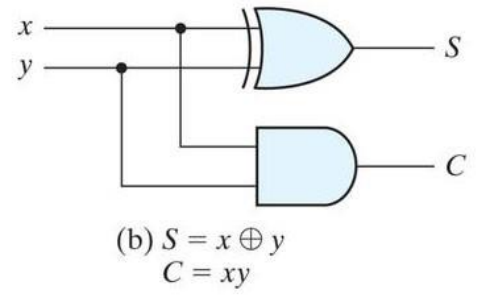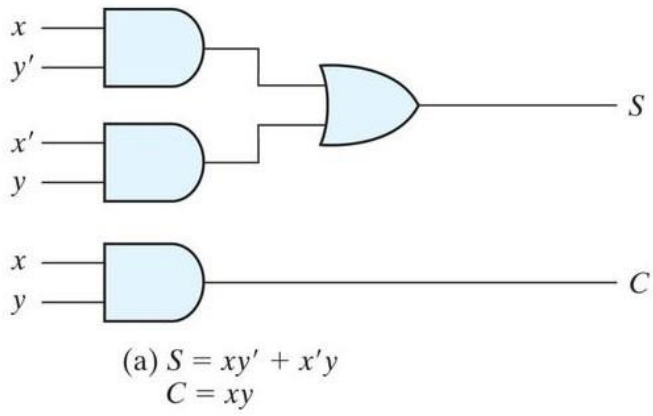


For S:

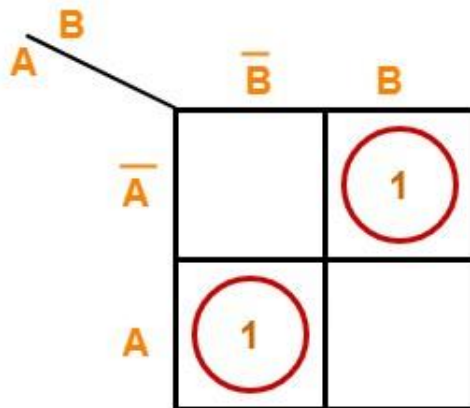

$$S = A \oplus B$$

For C:

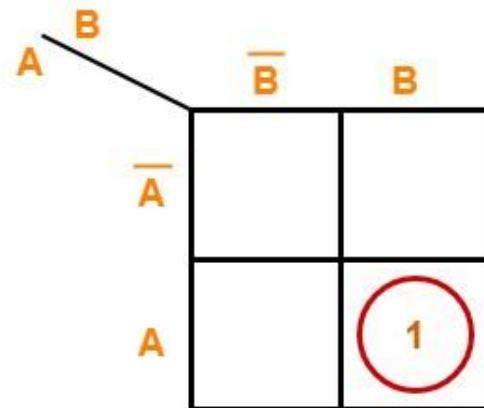

$$C = A \cdot B$$

K Maps

Adder

Design an Adder for 1-bit numbers?


1. Specification:

2 inputs (X,Y)
2 outputs (C,S)

2. Formulation:

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

3. Optimization/Circuit

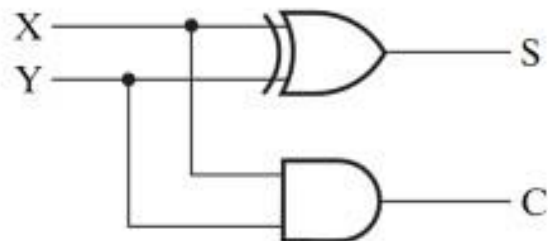

Full Adder

A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum		YZ			
X		00	01	11	10
	0	0	1	0	1
	1	1	0	1	0

Carry		YZ			
X		00	01	11	10
	0	0	0	1	0
	1	0	1	1	1

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

$$= X \oplus Y \oplus Z$$

$$C = XY + YZ + XZ$$

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

FIGURE 4.6 K-Maps for full adder

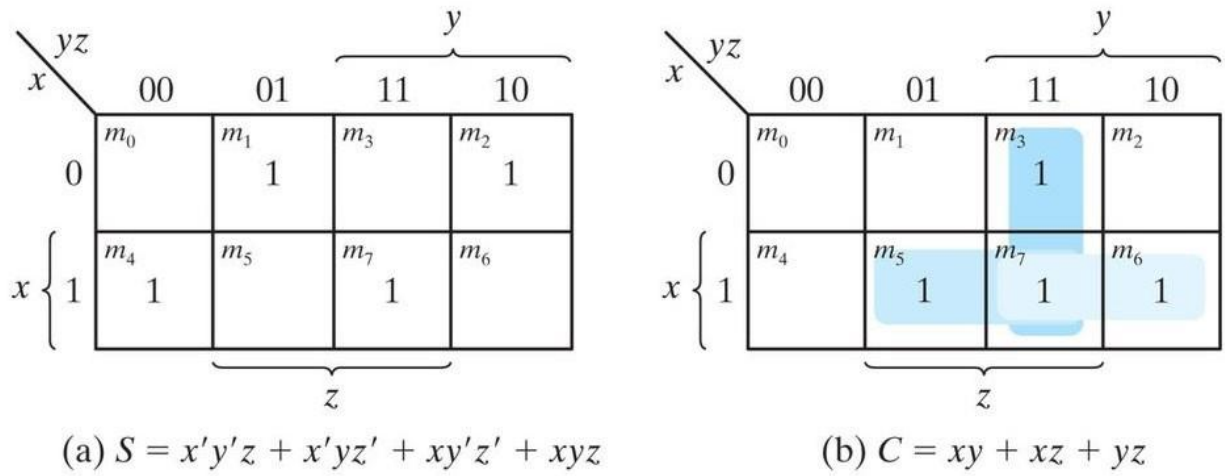


FIGURE 4.7 Implementation of full adder in sum-of-products form


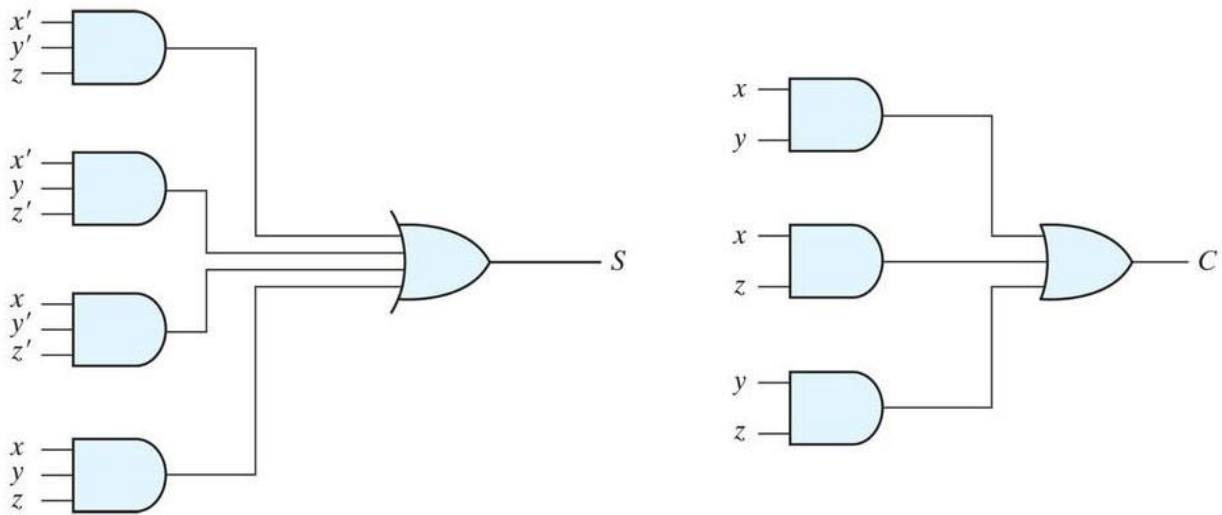


FIGURE 4.8 Implementation of full adder with two half adders and an OR gate

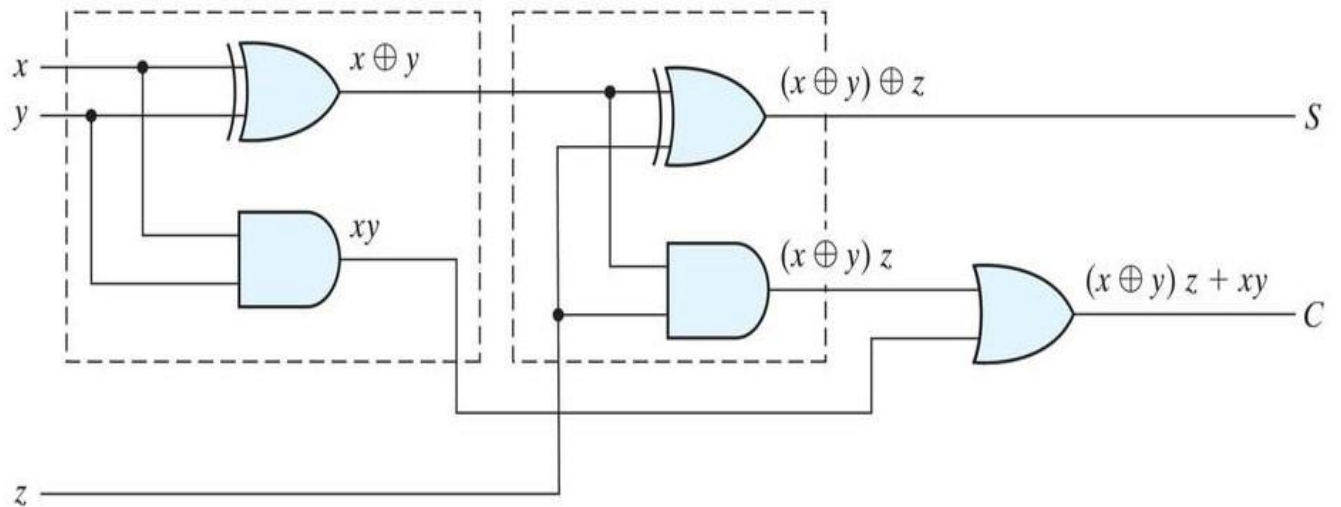

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$

$$C = XY + XZ + YZ$$

$$= XY + XYZ + XY'Z + X'YZ + XYZ$$

$$= XY(1 + Z) + Z(XY' + X'Y)$$


$$= XY + Z(X \oplus Y)$$

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$
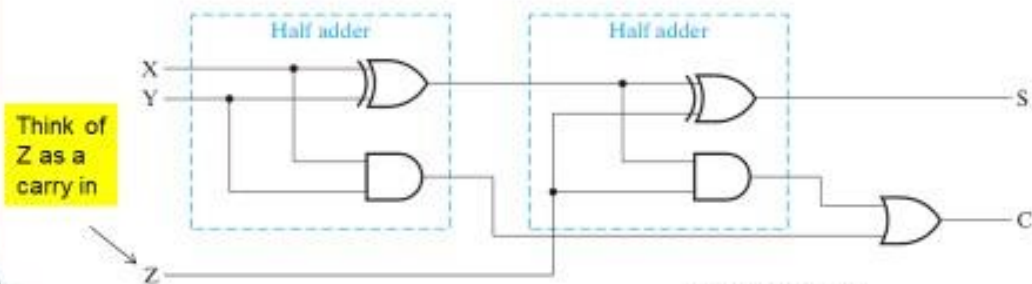
$$C = XY + XZ + YZ = XY + Z(X \oplus Y)$$




Src: Mano's Book

Binary Subtractors (Half and full Subtractor)



$$D = \overline{A}.B + A.\overline{B}$$

$$B_o = \overline{A}.B$$

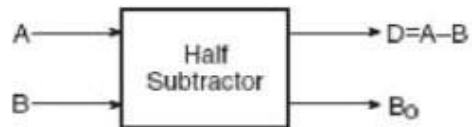


A	B	D	B _o
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Half Subtractor

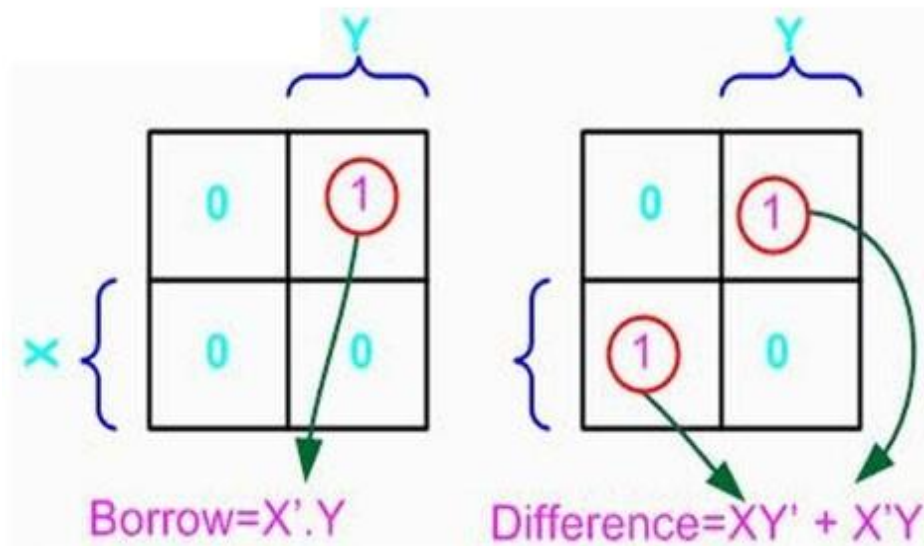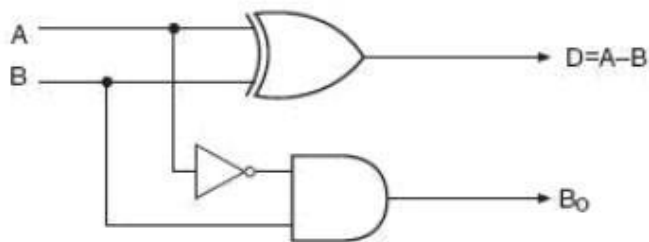

Full Subtractor

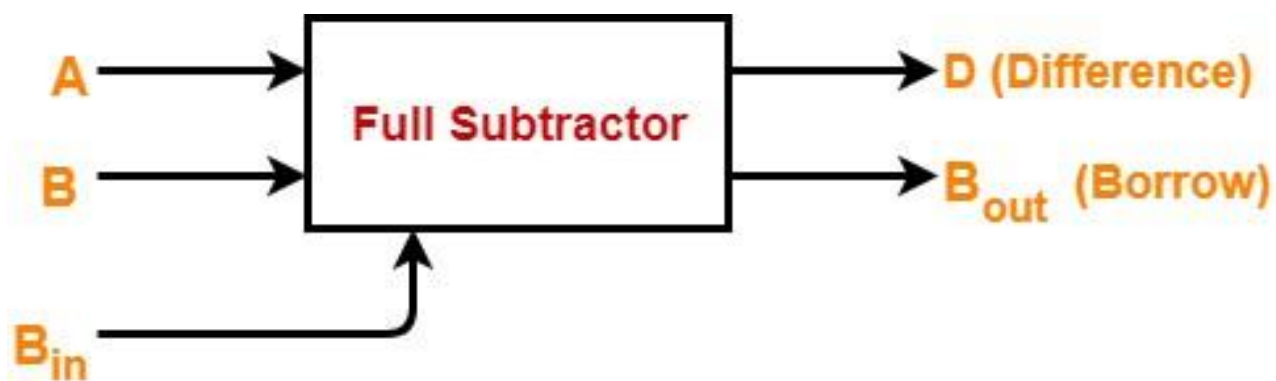

Full Subtractor-Truth Table				
Input			Output	
A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

For D

A \ BB _{in}				
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$D = \overline{A}\overline{B}B_{in} + \overline{A}B\overline{B}_{in} + A\overline{B}\overline{B}_{in} + AB B_{in}$$

For B_{out}

A \ BB _{in}				
	00	01	11	10
0	0	1	1	1
1	0	0	1	0

$$B_{out} = \overline{A}B_{in} + \overline{A}B + BB_{in}$$

Fig. 3.21 Maps for full-subtractor

$$\begin{aligned}
 \text{Difference} &= \overline{A} \overline{B} C + \overline{A} B \overline{C} + A \overline{B} \overline{C} + ABC \\
 &= C (\overline{A} \overline{B} + AB) + \overline{C} (\overline{A} B + A \overline{B}) \\
 &= C (A \odot B) + \overline{C} (A \oplus B) \\
 &= C (\overline{A \oplus B}) + \overline{C} (A \oplus B) \\
 &= C \oplus (A \oplus B)
 \end{aligned}$$

