

# DIGITAL LOGIC DESIGN



## Lab Manual – 02

Topic:

1. DeMorgan's Theorem and its implementation in Boolean algebra

<b>Course Instructor:</b>	<b>Mr. Tariq Mehmood Butt</b>	<a href="mailto:tariq.butt@pucit.edu.pk">tariq.butt@pucit.edu.pk</a>
<b>Teacher Assistants:</b>	Hafiz Muhammad Ahmad	<a href="mailto:bcsf21m502@pucit.edu.pk">bcsf21m502@pucit.edu.pk</a>
	Syed Muhammad Zain Raza Zaidi	<a href="mailto:bcsf21m510@pucit.edu.pk">bcsf21m510@pucit.edu.pk</a>
	Zahra Malik	<a href="mailto:bcsf21m550@pucit.edu.pk">bcsf21m550@pucit.edu.pk</a>
	Bilal Ahmad	<a href="mailto:bsdsf21m022@pucit.edu.pk">bsdsf21m022@pucit.edu.pk</a>

## 1) Demorgan's Theorem:

De Morgan's Theorem, is a powerful tool in digital design. The theorem explains:

1. the complement of the product(AND) of all the terms is equal to the sum(OR) of the complement of each term.

$$(A.B.C. \dots)' = A' + B' + C' + \dots$$

2. The complement of the sum(OR) of all the terms is equal to the product(AND) of the complement of each term.

$$(A+B+C+ \dots)' = A'.B'.C'. \dots$$

Therefore,

According to De Morgan's theorem,

1. A NAND gate is equivalent to an OR gate with **inverted** inputs.
2. A NOR gate is equivalent to an AND gate with **inverted** inputs.

### NAND



$$Y = \overline{AB} = \overline{A} + \overline{B}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

### NOR



$$Y = \overline{A+B} = \overline{A} \overline{B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

### Lab Tasks:

1. Prove the following identities:
  - a.  $A'B' = (A+B)'$
  - b.  $A'+B' = (A.B)'$
2. Implement NOR gate using NAND gate.
3. Implement NAND gate using NOR gate.

### Home Task:

Circuit diagrams of implementations of all gates using NAND and NOR gates separately.

### Instructions:

- **Show your work:** Make sure you have shown your work to respective TA in the lab before leaving it.
- **Clean Up Workspace:** Ensure your workstation is clean and organized. Clear away any papers, or materials used during the lab session.
- **Turn Off Equipment:** Power down all equipment.
- **Secure Components:** Place all physical components such as wires, ICs at their designated places. Do not leave components lying around on the workbench.
- **Return Borrowed Equipment:** Return the ICs and other equipment taken from server room.
- **Save Work:** Follow the instruction given in the lab regarding saving your work.
- **Dispose of Waste:** Dispose of any non-recyclable items, in the designated waste bins. Recycle any recyclable materials according to lab guidelines.
- Follow any additional instructions provided by the lab instructor or TAs regarding lab cleanup and departure procedure.
- Do the home task on sheets, and submit it in the Google Classroom. The name of your file must be YourRollNumber\_HTLab02.pdf
  - (i.e. BCSF23M5XX\_HTLab02.pdf/ BSDSF23XXXX\_HTLab02.pdf).