Lab 06 Home Task
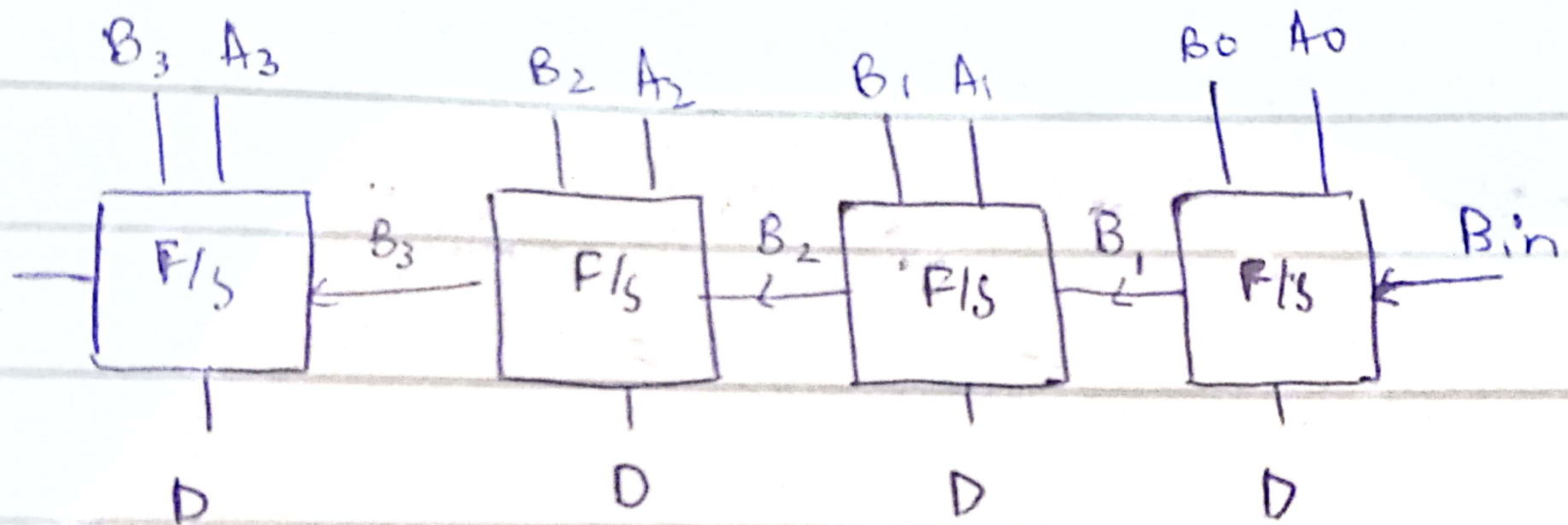

4-bit subtractor
using 4 full substractor